
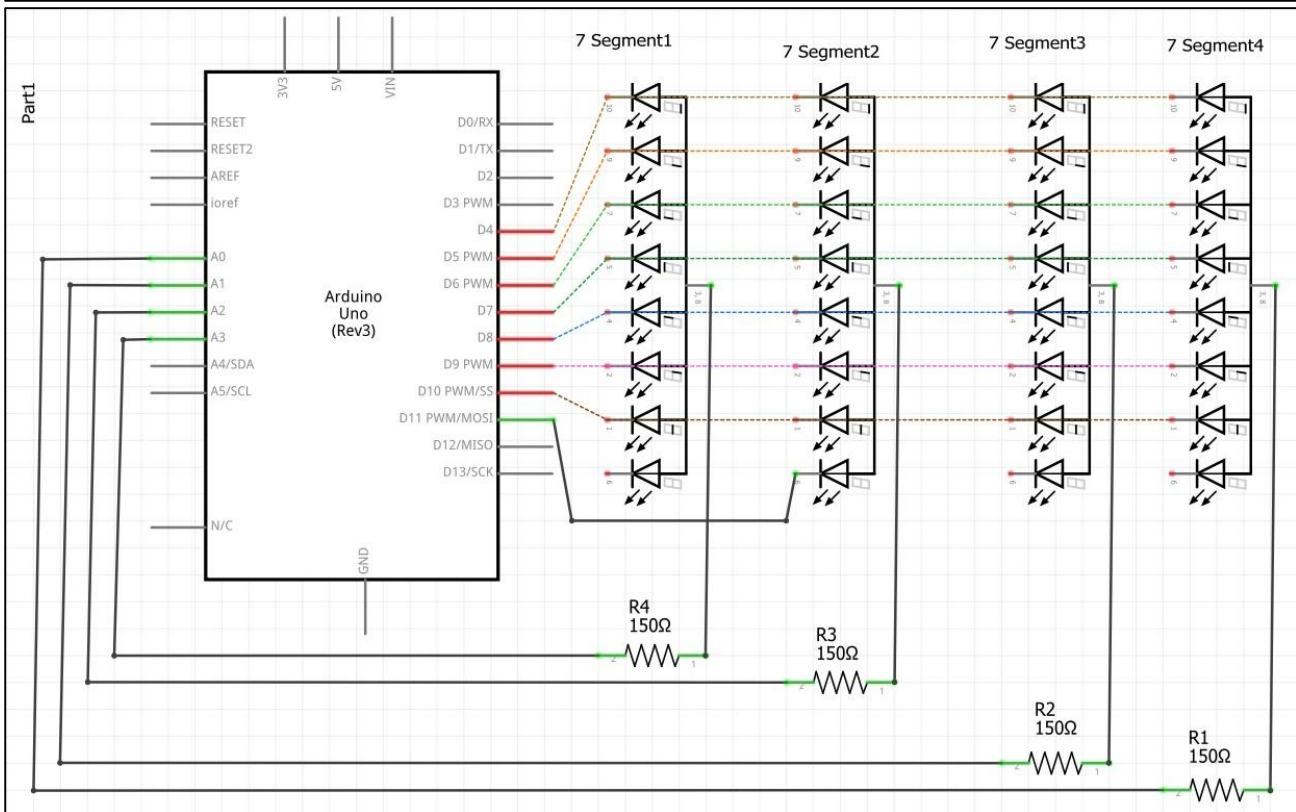


SETR

Practice part 2

Circuit schemes:

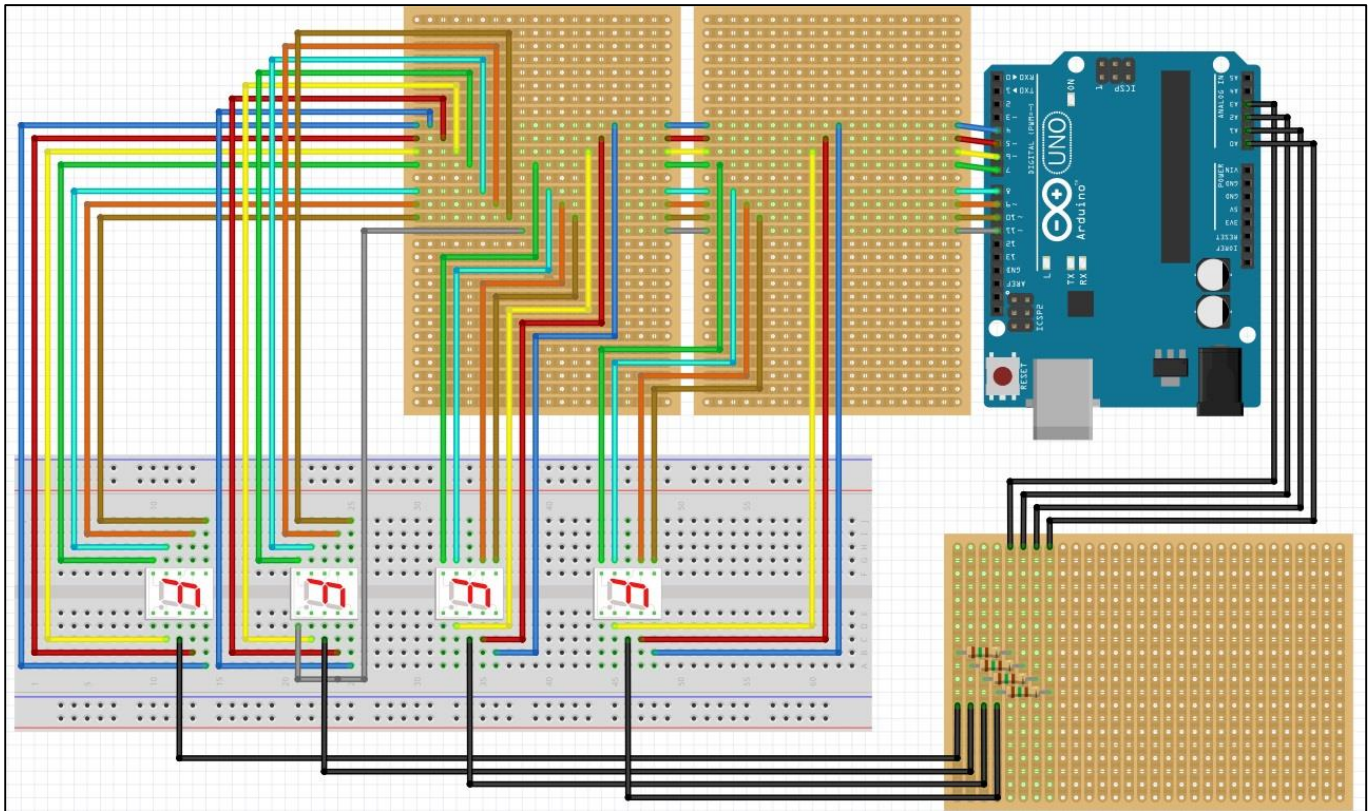

This scheme works for all practice exercises. So, we have 4 LEDs. As we see identical pins on LEDs are connected parallel. Then grounds of our LEDs are connected to analog pins A0-A3.